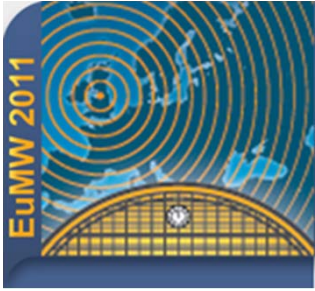





Universality in the Large Signal Behaviour of Varactor Junctions

Prof. J David Rhodes, Isotek



Semiconductor Varactors

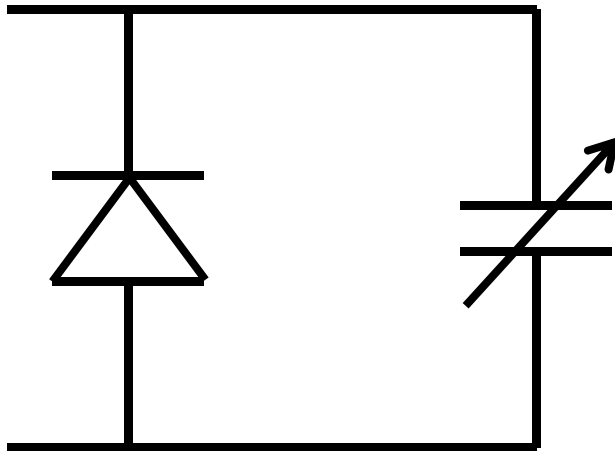

T_1 = Time constant of carrier recombination

T_2 = Period of fundamental signal

CASE A

$$T_1 \ll T_2$$

CASE B

$$T_1 \gg T_2$$



Conjectures


CASE A

Within the constraints of the network within which it is embedded, for a given incident power level supplied at the fundamental frequency, the DC voltage developed across the varactors will always be minimised.




CASE A

VOLTAGE

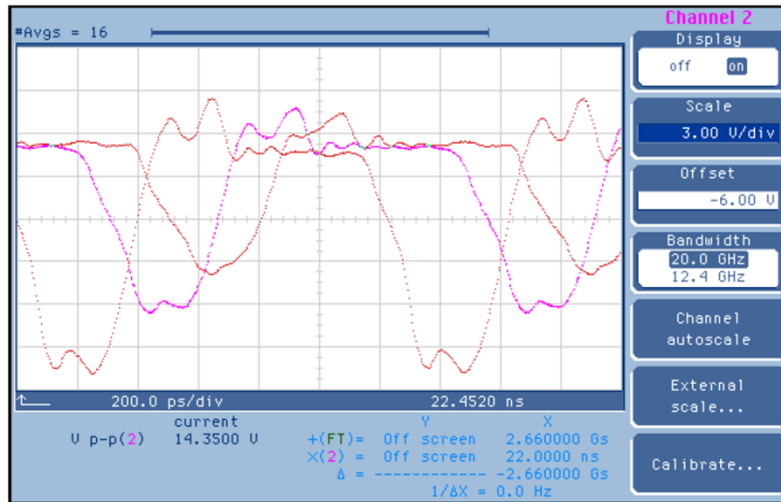

Pin - relative dBm	CW Frequency MHz	Fundamental dBm	F2 dBm	F3 dBm	F4 dBm	F5 dBm	F6 dBm	F7 dBm	File
-14	806	21.3	17.6	3.8	-5.4	-5.8	-8	0	I587
-12.5	811	24.1	20.0	6.6	-2.3	-0.2	+2	+1.5	I589
-11	822.85	26.4	21.8	7.3	+2.0	+5.5	+4.0	-15	I590

SPECTRUM

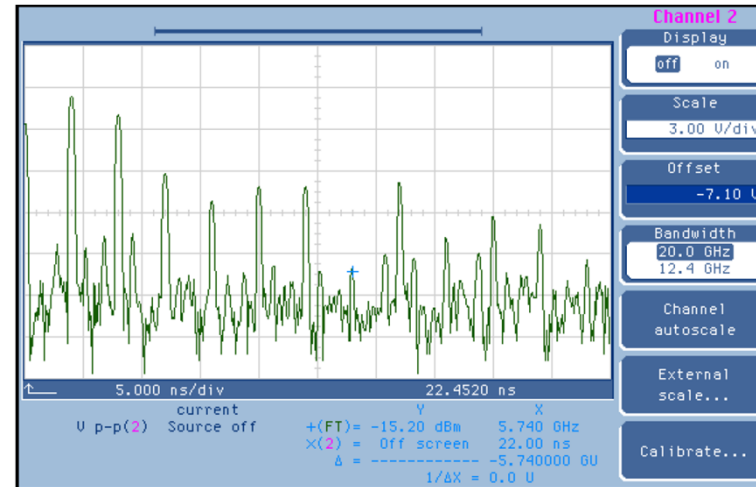


Measured voltage of spectrum and gate circuit of a GaAs pHEMT with open circuits at harmonics

$$V_{DC} = \frac{V_{RF}}{2 \cos\left(\frac{\pi}{n+2}\right)} \quad \text{with zeros at } \theta_r = \sin\left[\frac{(2r-1)\pi}{n+2}\right] \quad \text{where } r = 1 \rightarrow n$$

$$V_{max} = \frac{2 \cot^2\left(\frac{\pi}{2(n+2)}\right)}{n+2} \cdot V_{DC}$$



Case B: Experimental Setup

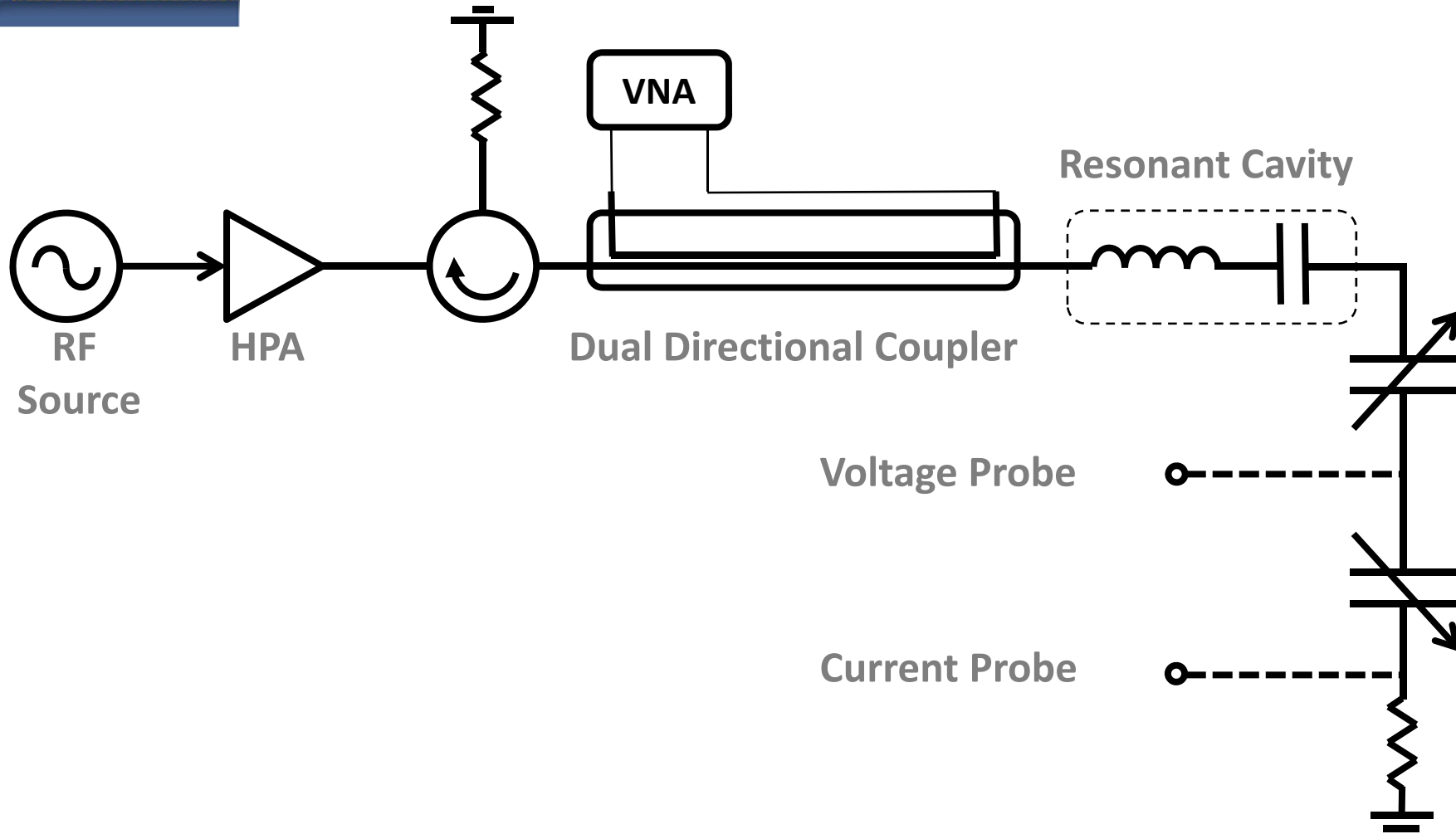



Conjectures



CASE B

Within the constraints of the network within which it is embedded, for a given incident power level supplied at the fundamental frequency, the current limits and the amount of sub-harmonic energy oscillating between the varactors will always be maximised.



CASE B: PN Junction Varactors Type 1 : Abrupt Junction

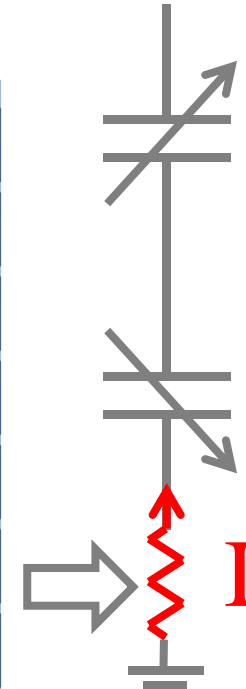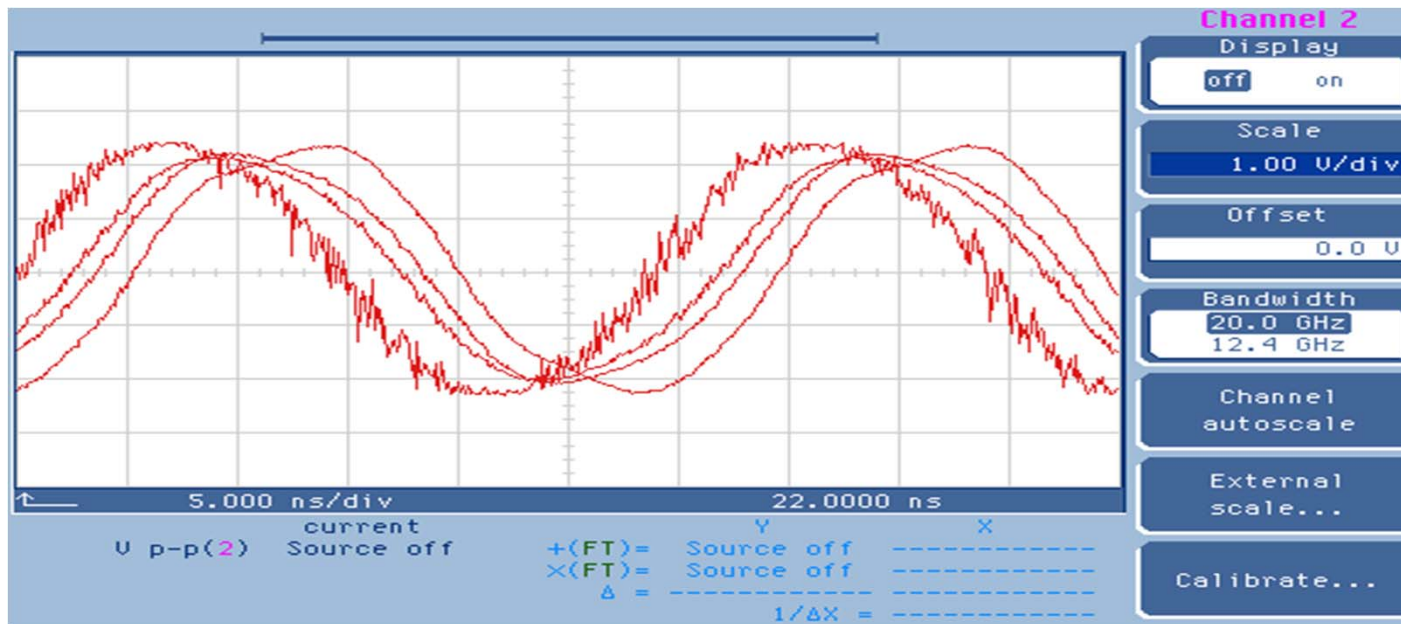Current measurement at varying power levels




Pin	Pdc (centre tap voltage)	f0(dBm)	2f0(dBm)	3f0(dBm)	4f0(dBm)	5f0(dBm)
4.5	12.9	22.5	-22	.5	-15	-10.2
2.45	11.4	22.3	-20	-.5	-40	-40
1.14	6.3	22.1	-20	-6	-40	-40
0.44	2.1	21.8	-40	-4.5	-40	-40





CASE B: PN Junction Varactors

Type 1 : Abrupt Junction

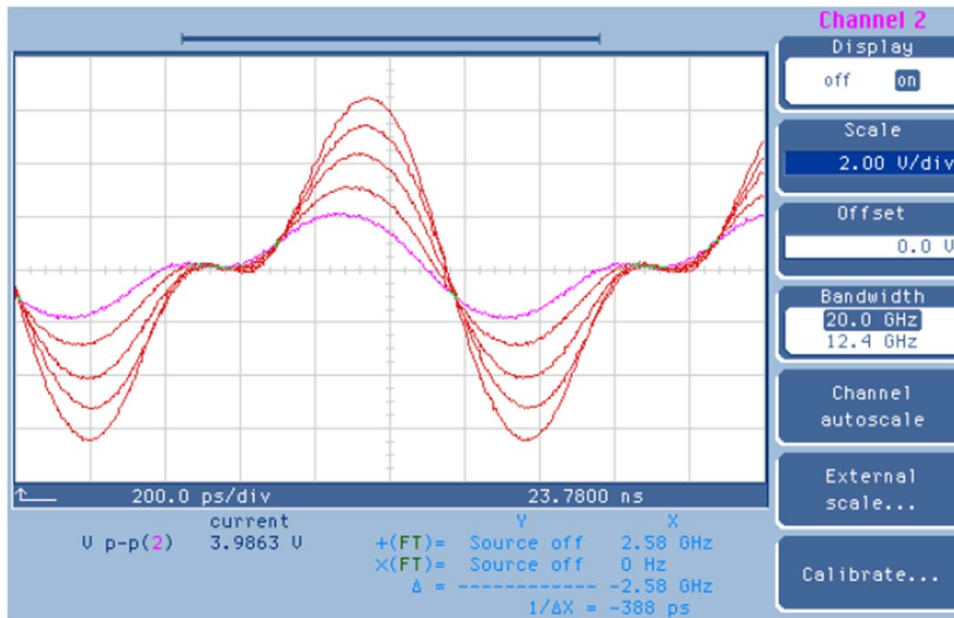

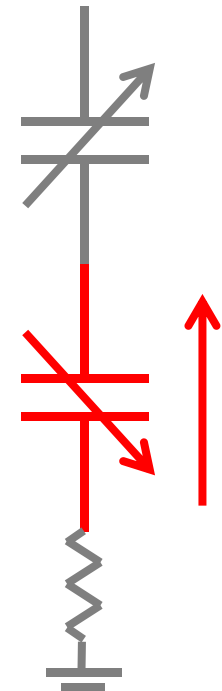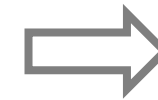Voltage across single device at various power levels



$$V_{pp} = V_{DC}$$

dBc	Volts	dBc			
		f0(dBm)	2f0(dBm)	3f0(dBm)	4f0(dBm)
8.3	12.3	22.8	18.3	-0.5	-7
6.36	11.6	22.65	17.0	0	-9
4.0	9.16	20.25	13.5	-2.5	-8.7
2.2	6.33	16.7	10.0	-5.6	-11.3
1.16	4.2	12.8	6.2	-9.8	-14



Instantaneous Power

P = Instantaneous Power Extracted from bottom device

$$P \propto -\sin\theta \cos\theta (1 + \varphi \cos\theta)$$

Where

$$I \propto -\cos\theta$$

$$V \propto \sin\theta (1 + \varphi \cos\theta)$$



Instantaneous Energy

Bottom Device

$$E \propto \frac{\cos^2 \theta}{2} \left(1 + \frac{2\varphi}{3} \cos \theta \right) \geq 0$$



Top Device


$$E \propto \frac{\cos^2 \theta}{2} \left(1 - \frac{2\varphi}{3} \cos \theta \right) \geq 0$$





Energy Function
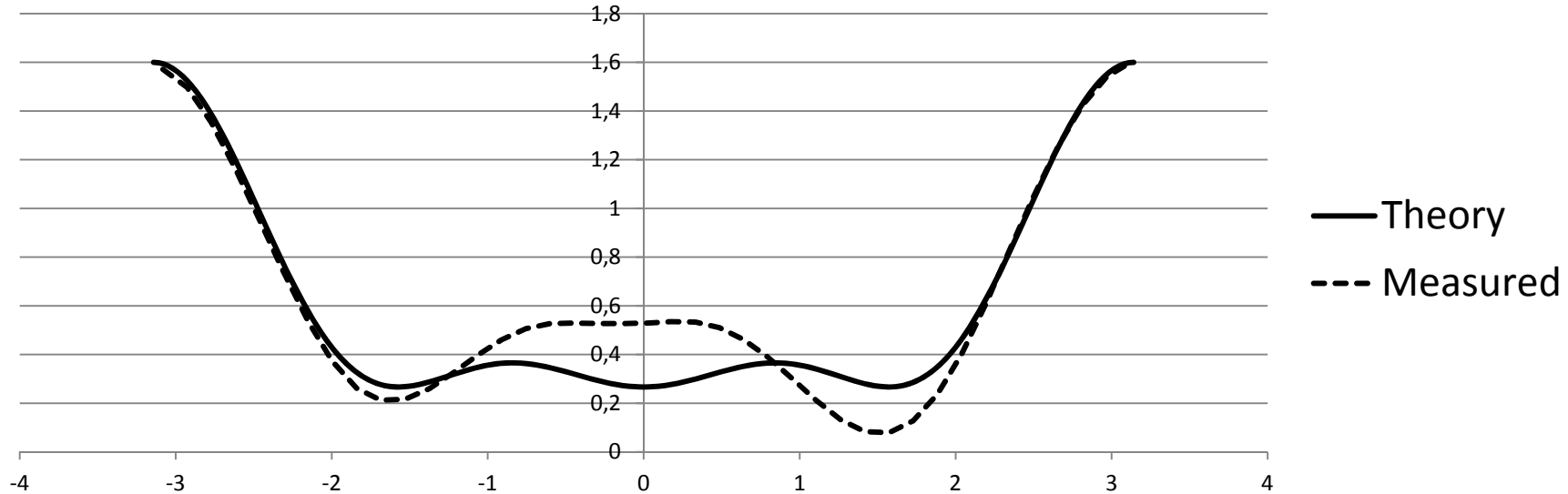
$$E \propto \frac{\cos^2 \theta}{2} (1 + \cos \theta)$$






CASE B: PN Junction Varactors Type 2 : Hyper - Abrupt Junction

Initially, additional inductance was added in series with the devices to ensure that no third harmonic current could flow.



The measured current was approximately sinusoidal and the measured voltage was

$$V_{pp} = V_{DC}$$

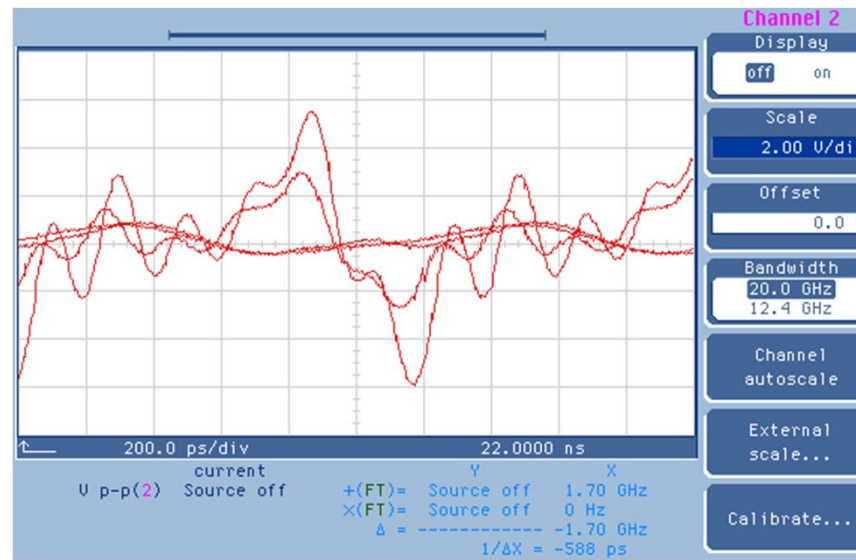

Pin	Pdc	f0	2f0	3f0	4f0	5f0	6f0
3.7	11.1	15.0	16.9	4.8	-6.7	6.2	13.3
2.12	5.7	2.0	9.4	-6.3	-4.4	-13.0	0
1.68	2.58	1.8	-1.0	-	-23	-17	-
1.11	1.53	2.85	-7	-	-	-	-




CASE B: PN Junction Varactors Type 2 : Hyper - Abrupt Junction

Hence, the energy function will be of 4th degree of the form:

$$E \propto 1 + A \cos\theta + B \cos 2\theta + C \cos 3\theta + D \cos 4\theta$$

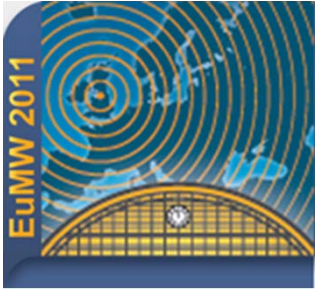*If this is zero with turning points at $\theta_1, \theta_2, 2\pi - \theta_1, 2\pi - \theta_2$ and chosen such that A is maximised, the solution is **singular!***



CASE B: PN Junction Varactors Type 2 : Hyper - Abrupt Junction

Let $\theta_1 = \frac{\pi}{2}$ and $\theta_2 = \frac{5\pi}{6}$, then

$$\theta = \frac{\pi}{2} \quad 1 - B + D = 0 \quad \text{Equation 1}$$

$$\theta = \frac{5\pi}{6} \quad 1 - \frac{\sqrt{3}}{2}A + \frac{B}{2} - \frac{D}{2} = 0 \quad \text{Equation 2}$$

Dividing Equation 1 by 2 and adding to Equation 2 gives
 $A = \sqrt{3}$ which is the stationary maximum solution

Hence,

$$E \propto \cos^2\theta \left(\frac{\sqrt{3}}{2} + \cos\theta \right)^2$$


with $I \propto -\cos\theta$

$$V \propto \frac{3}{2}\sin\theta + \frac{3\sqrt{3}}{2}\sin 2\theta - \sin 3\theta$$



CASE B: PN Junction Varactors Type 2 : Hyper - Abrupt Junction


...and the measured value of energy is :

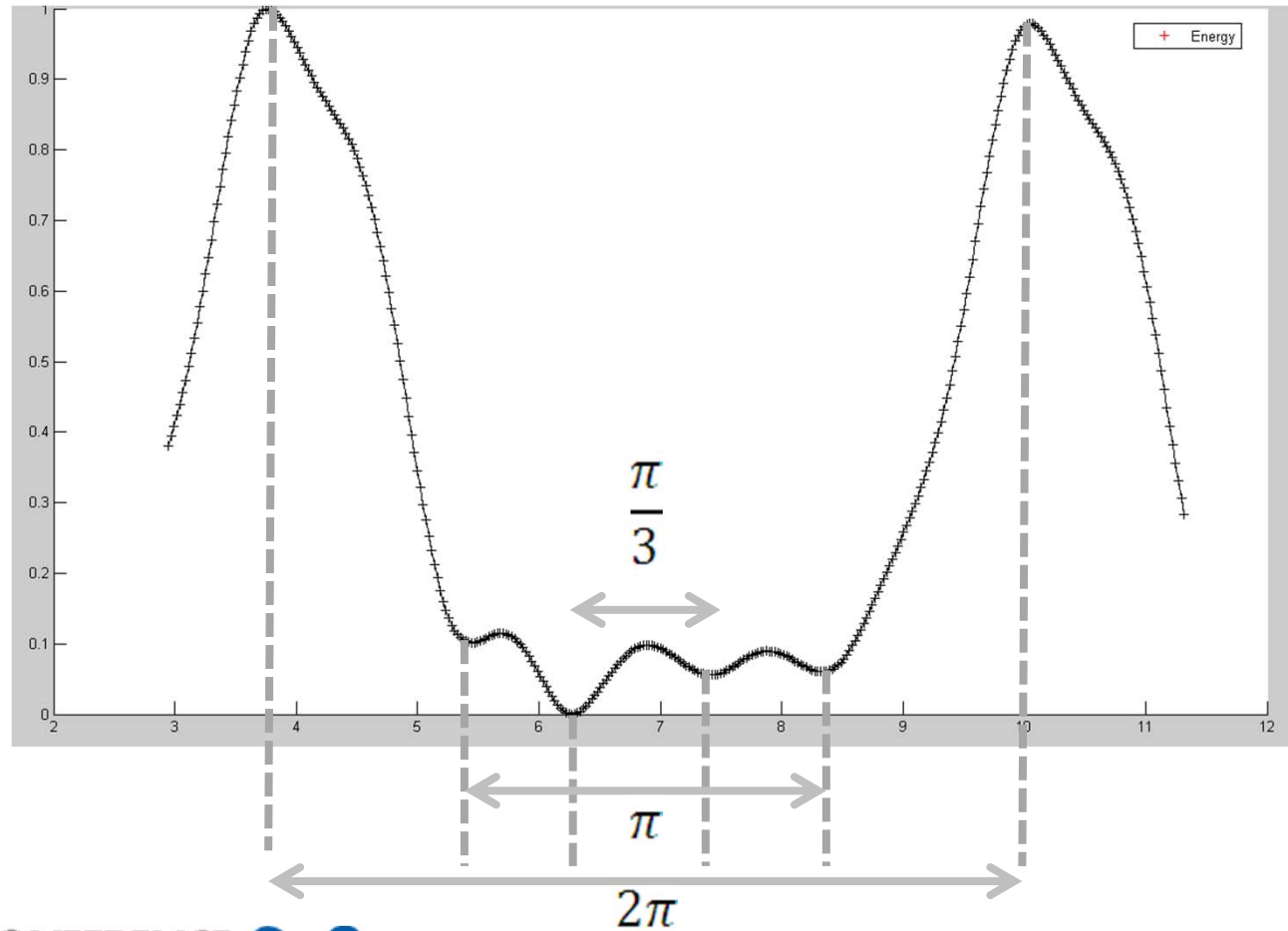



Hyper Abrupt with Finite Reactance at the 3rd Harmonic

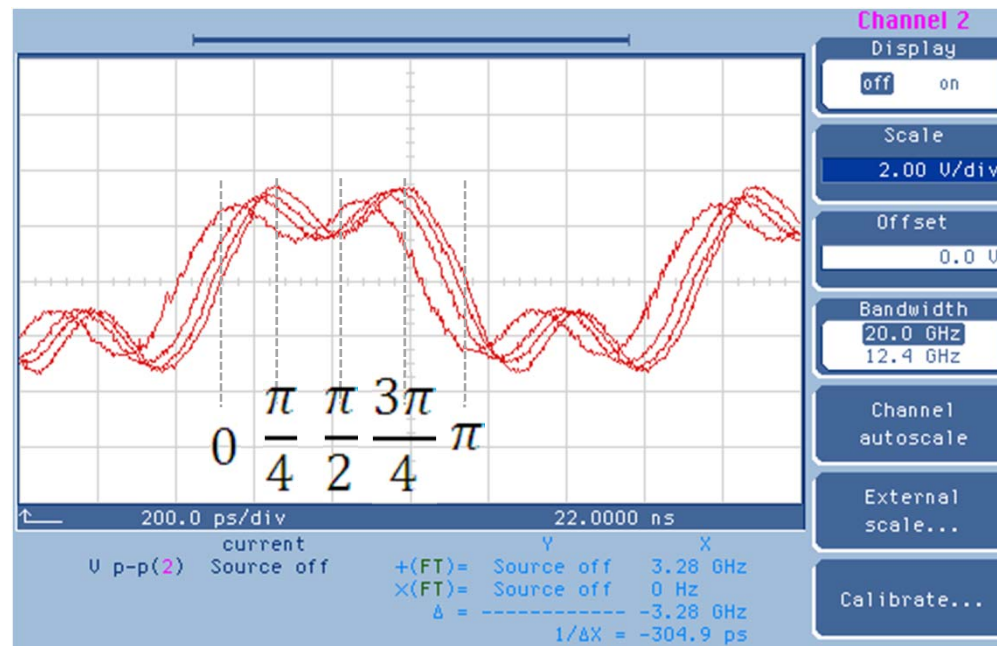Removing the series inductor produces a measured current of:



Constant current at different power levels of 0,-3,-6,-12 dB



Hyper Abrupt with Finite Reactance at the 3rd Harmonic

Hence,

$$I \propto -\left(\cos \theta - \frac{1}{3}\cos 3\theta\right)$$

$$\frac{dI}{d\theta} = 0 \text{ at } \cos^2 \theta = \frac{1}{2}$$

Thus, $E_V \cdot E$ may be expressed as :

$$\text{Even } (E) \propto (1 + A \cos 2\theta)^2 (6A + 1 - 2A \cos 2\theta)$$

with,

$$\frac{dE}{d\theta} = P \propto -12A^2 \sin 2\theta (1 + A \cos 2\theta) (2 - \cos 2\theta)$$



Hyper Abrupt with Finite Reactance at the 3rd Harmonic

with,

$$I \propto -\cos \theta (2 - \cos 2\theta) = -\frac{3}{2}(\cos \theta - \frac{1}{3} \cos 3\theta)$$

and

$$\begin{aligned} V &\propto \sin \theta (1 + A \cos 2\theta) \\ &= \left(1 - \frac{A}{2}\right) \sin \theta + \frac{A}{2} \sin 3\theta \end{aligned}$$



Hyper Abrupt with Finite Reactance at the 3rd Harmonic

Hence,

$$\text{Input energy at fundamental frequency} \propto A^2 \left(1 - \frac{A}{2}\right) = E_1$$

and

$$\text{Output energy from 3rd harmonic termination} \propto \frac{A^3}{6} = E_3$$

Energy in lower device is :

$$E \propto (1 + A \cos 2\theta)^2 (6A + 1 - 2A \cos 2\theta) + K \\ + \varphi \cos^3 \theta \left(1 - \frac{2}{5} \cos^5 \theta\right) \geq 0$$



Hyper Abrupt with Finite Reactance at the 3rd Harmonic

$$P \propto -\sin 2\theta (2 - \cos 2\theta) \left(12 A^2 (1 + A \cos 2\theta) + \frac{\varphi}{2} \cos \theta \right)$$

If zero at $\theta = \theta_0$, then

$$\varphi = \frac{-24A^2(1 + A \cos 2\theta_0)}{\cos \theta_0}$$

To be maximum and stationary, φ must have the same dependence as E_1



Hence $\theta_0 = \frac{2\pi}{3}$ and

$$\varphi = 48 A^2 \left(1 - \frac{A}{2}\right)$$

For E to be zero at $\theta = \theta_0$

$$K = \frac{-89 A^3 + 243 A^2 - 120 A - 20}{20}$$

and is a stationary when

$$A = 1.5256$$

Hence


$$V \propto \left(1 - \frac{A}{2}\right) \sin \theta + \left(1 - \frac{A}{2}\right) \sin 2\theta + \frac{A}{2} \sin 3\theta$$

$$\approx \propto \sin \theta + \sin 2\theta + 3.2 \sin 3\theta$$



Hyper Abrupt with Finite Reactance at the 3rd Harmonic

Measured Voltage at Varying Power Levels

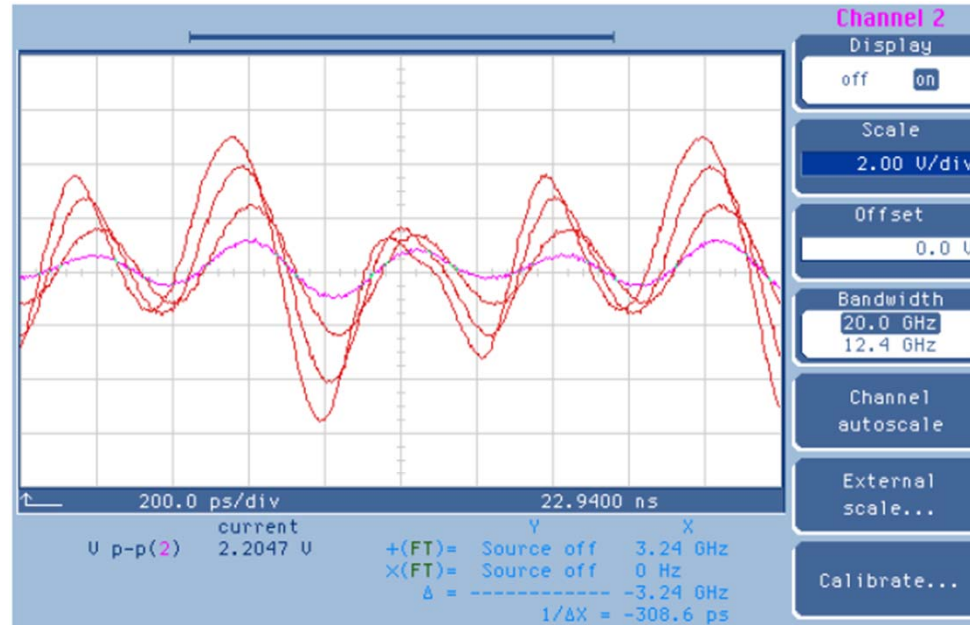

dBc	Volts	dBc				
		f ₀	2f ₀	3f ₀	4f ₀	5f ₀
Pin	V _{dc}					
9.0	7.6	12.3	10.2	19.15	-40	1
5.07	4.8	7.9	7.7	18.0	-40	-2.8
2.93	3.8	2.9	4.8	14.9	-20	-18
1.47	2.6	-13.9	0	5.9	-20	-23


$$V_{pp} = V_{DC}$$




Energy Function in both Varactors



THEORY

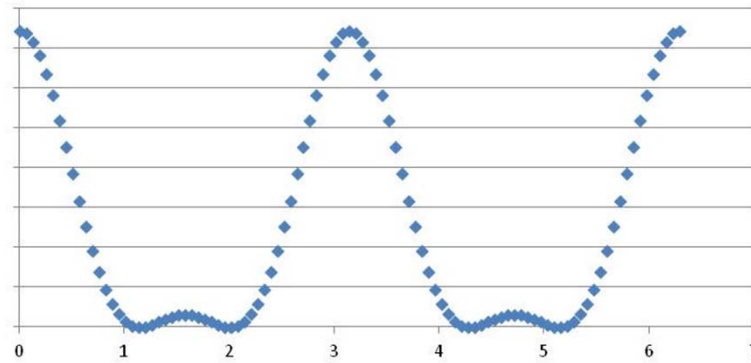


MEASURED

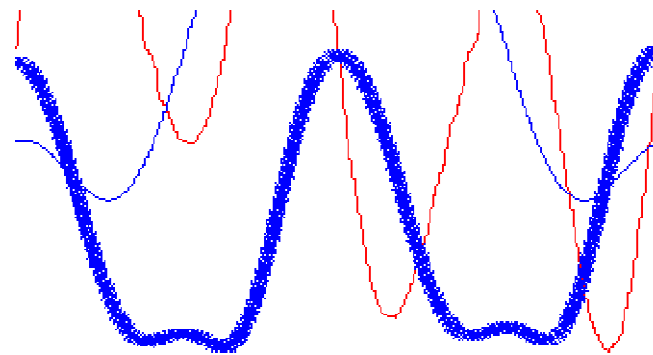




Comparison of Theoretical and Measured – Single Device

THEORY

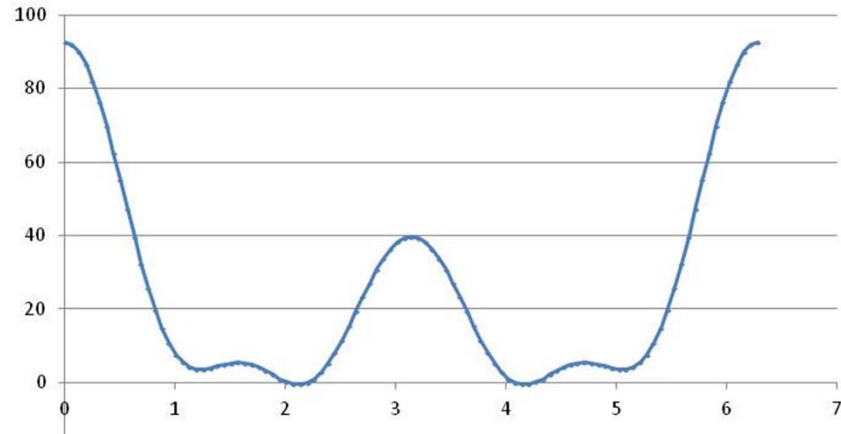


MEASURED

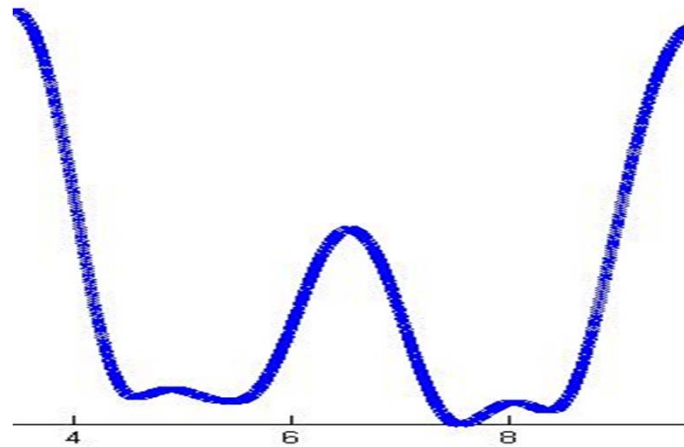



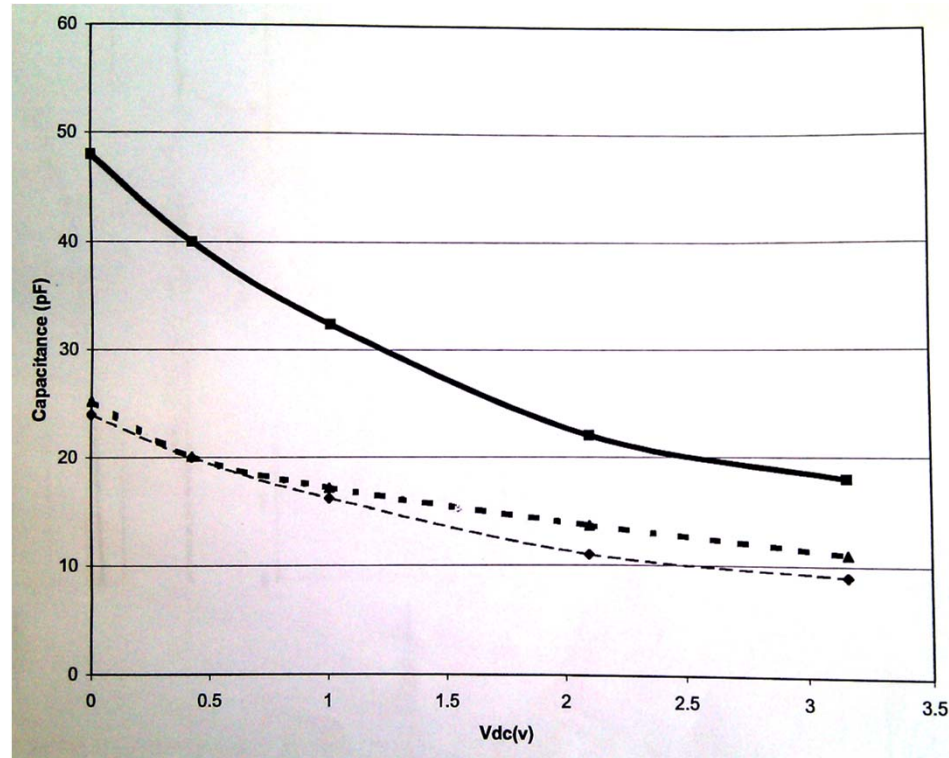
Measured Effective Capacitance at Fundamental



Third harmonic energy stored in external reactance
 \approx energy stored at fundamental in devices



Equivalent Circuit of Varactor Pair

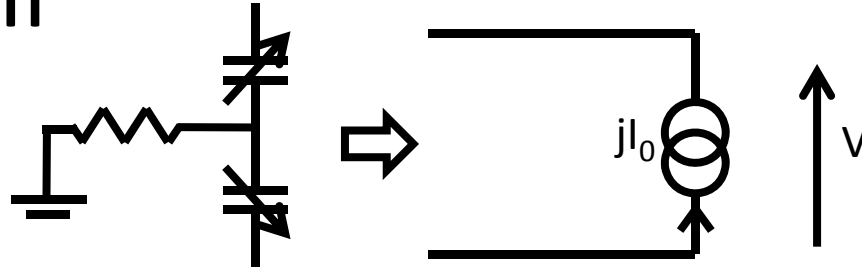


- **Constant current generator**
 - Constrained such that voltage is always at 90° to the constant current generator

- N.B. Some resistance has to be added at the common junction to discharge the DC voltage at $>$ modulation rate of the signals



Typical Application for PA

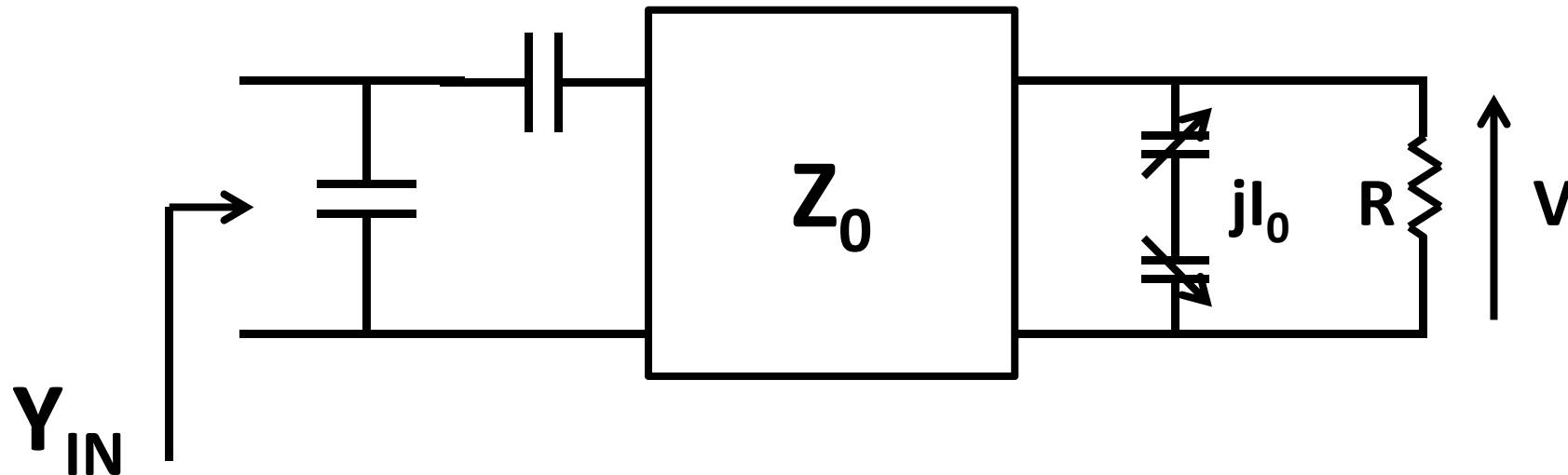

Output circuit for power amplifier producing an approximately constant level of voltage at the input to provide high efficiency over a high dynamic range



Conclusion 1

For large signals across varactor diodes, the non-linear equation

$$I = C(V) \frac{dV}{dt}$$

Is **NOT** valid



Conclusion 2

For PN junction devices, over many RF cycles, the behaviour is totally governed by the sub-harmonic energy oscillating between the back to back devices which is maximised within the constraint of the network in which it is embedded.



Conclusion 3

Assuming discharge is accomplished at the signal modulation rate, the equivalent circuit is simply a current generator constrained by the phase of the voltage across it always being at 90° to the current.



Conclusion4

Opens up a whole new field in non-linear circuit theory



Acknowledgements

The author would like to thank Dr. Mike Roberts of Slipstream Design for all the experimental work which was difficult, and for the preparation of these slides